 


3. Implement the *power_on* module according to the spec below:


Port	Direction	Width	Description
resetb	In	1	Asynchronous active low reset
clk	In	1	Clock at 100Mhz
power_good	In	1	Power good indication
enable	Out	1	Enable signal. The <i>enable</i> should be asserted 300ns after <i>power_good</i> signal is asserted and stable



The Implementation should include:

- (5 points)** Block Diagram of the *power_on* module
- (10 points)** SystemVerilog code (*power_on.sv*)
- (15 points)** Testbench (*power_on_tb.sv*) that
 - Print a message with the delay between the 2 signals
 - Print error message if the *enable* rise less than 300ns after the *power_good* rising - based this checker on “**fork-join**” construct.

Fail

 

4. (50 points) Binary GCD Algorithm

Implement the Euclidean algorithm “Greatest Common Divisor” (GCD) according to the following spec:

Pin name	Direction	Description
clk	In	100MHz clock
resetb	In	Asynchronous active low reset
u[7:0]	In	Unsigned, greater than 0 number
v[7:0]	In	Unsigned, greater than 0 number
ld	In	1 cycle pulse which tells that new u and v are ready and stable Assumption: time between 2 load pulses is long enough. New load will come only after previous calculation was finished.
res[7:0]	out	gcd(u,v) - Great Common Divisor of u and v. for example: if u = 36 and v = 24 res = 12 (after certain amount of cycles. there is no constraint on calculation speed) During the GCD calculation res = 0.
done	out	Indicate that the result at res[7:0] is valid (active high until the next load operation)

The GCD algorithm:

While ($u \neq v$) :

- a) If both, u and v , are even: $\text{gcd}(u,v) = 2 * \text{gcd}(u/2, v/2)$
- b) If only u is even: $\text{gcd}(u,v) = \text{gcd}(u/2, v)$
If only v is even: $\text{gcd}(u,v) = \text{gcd}(u, v/2)$
- c) If both, u and v , are odd:
 - if ($u > v$) $\text{gcd}(u,v) = \text{gcd}(u-v, v)$
 - if ($v > u$) $\text{gcd}(u,v) = \text{gcd}(u, v-u)$

The GCD result is $u * 2^n$

while n is the number of times that both u and v were even (case a.)

The Implementation should include:

- a) **(10 points)** Block Diagram of the GCD module
- b) **(30 points)** SystemVerilog code (**gcd.sv**)
- c) **(10 points)** A testbench (**gcd_tb.sv**) with a random test that is repeated 100 times. The test should display a message like: GCD (24,36) = 12 and response with error message if needed. For the golden model, implement a function that calculates the expected results using the regular Euclidean algorithm.